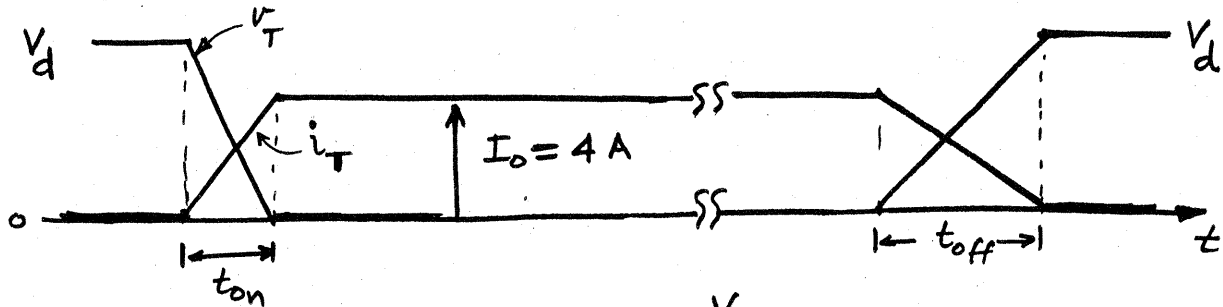


Problem 2-2



$$I_o = \frac{V_d}{R} = \frac{300}{75} = 4.0 \text{ A}$$

$$t_{on} = t_{ri} + t_{fv} = 150 \text{ ns}$$

$$t_{off} = t_{rv} + t_{fi} = 300 \text{ ns}$$

$$0 < t < t_{on}$$

$$i_T = I_o \frac{t}{t_{on}}$$

$$V_T = V_d \left(1 - \frac{t}{t_{on}}\right)$$

$$\therefore (p_T)_{on} = V_d \frac{I_o}{t_{on}} \left(1 - \frac{t}{t_{on}}\right) t \quad \therefore (W_T)_{on} = \int_0^{t_{on}} (p_T)_{on} dt$$

$$\begin{aligned} \therefore (W_T)_{on} &= \frac{V_d I_o}{t_{on}} \int_0^{t_{on}} \left(1 - \frac{t}{t_{on}}\right) t \cdot dt \\ &= \frac{V_d I_o t_{on}}{6} \end{aligned}$$

Similarly,

$$(W_T)_{off} = \frac{V_d I_o t_{off}}{6}$$

$$\therefore (W_T)_{switching} = (W_T)_{on} + (W_T)_{off} = \frac{V_d I_o}{6} [t_{on} + t_{off}]$$

$$P_s = f_s (W_T)_{switching} = \frac{V_d I_o}{6} f_s [t_{on} + t_{off}]$$

avg. switching
power loss

$$\therefore P_s = \frac{300 \times 4}{6} \times 100 \times 10^3 [150 + 300] \times 10^{-9} \text{ W} = 9 \text{ Watts}$$

[at 100 kHz]

In this circuit, P_s is $1/3$ of that in Problem 2-1.